

References

Ryan Hou

2025-02-20

Table of contents

Preface	3
Resources	4
1 Introduction	5
1.1 Perspective	5
1.2 High Level Ideas	5
2 Circuit Basics	6
2.1 Important Constants	6
2.2 Common Unit Conversions	6
2.3 Charge, Voltage, Current, Power	7
2.3.1 Charge (Q)	7
2.3.2 Voltage (V)	7
2.3.3 Current (I)	7
2.3.4 Power (P)	8
2.4 Resistance, Capacitance, Inductance	8
2.4.1 Resistance (R)	8
2.4.2 Capacitance (C)	9
2.4.3 Inductance (L)	9
2.5 Electric Fields	9
2.6 KVL & KCL	10
2.6.1 Kirchhoff's Voltage Law (KVL)	10
2.6.2 Kirchhoff's Current Law (KCL)	10
2.7 Basic Circuit Configurations	10
2.7.1 Series Connections	10
2.7.2 Parallel Connections	11
2.8 Capacitor	11
2.9 Additional Topics Relevant to CMOS/VLSI	11
2.9.1 Small Signal Analysis	11
2.9.2 RC Networks	12
2.9.3 Noise and Signal Integrity	12
2.9.4 Semiconductor Physics Basics	12
2.10 PN Junctions	13
2.10.1 Built-in Potential	13

2.10.2	Depletion Region	13
2.10.3	Current-Voltage Relationship	13
2.10.4	Junction Capacitance	14
2.10.5	Temperature Effects	14
2.11	Note	14
3	High-level Overview	16
3.1	MOS Transistors	16
3.2	CMOS Logic	18
3.2.1	Pass Transistors, Transmission Gates	18
3.2.2	Tristates	18
3.2.3	Multiplexers	18
3.3	Sequential Circuits	18
3.3.1	Latches	18
3.3.2	Flip-Flops	18
3.4	Fabrication & Layout	18
3.4.1	Fabrication Process	18
3.4.2	Layout Design Rules	18
3.5	Design Partitioning	18
3.6	Architecture	18
3.7	Logic Design	18
3.8	Circuit Design	18
3.9	Physical Design	18
3.10	Design Verification	18
3.11	Fabrication, Packaging, and Testing	18
4	CMOS Basics	19
4.1	MOS Transistor Basics	19
4.1.1	Silicon Lattice	19
4.1.2	PN Junction	20
4.1.3	Transistor Structure	22
4.1.4	Very Simplified Model	27
4.2	Long-Channel I-V Characteristics	31
4.3	C-V Characteristics	31
4.4	Nonideal I-V Effects	31
4.5	DC Transfer Characteristics	31
4.6	Resources / References	31
5	CMOS Fabrication & Process Technology	32
6	CMOS Capacitance	33
7	Inverters and More Gates	34

8 Delay	35
9 Power	36
10 Interconnect	37
11 Robustness	38
12 Circuit Simulation	39
13 Combinational Circuit Design	40
14 Sequential Circuit Design	41
15 Datapath Subsystems	42
16 Array Subsystems	43
17 Special-Purpose Subsystems	44
18 Design Methodology and Tools	45
19 Testing, Debugging, and Verification	46
20 Summary	47
21 Interview & Problems	48
21.1 Interview	48
21.2 Problems	48
21.2.1 CMOS	48
21.2.2 Logic Design	48
References	49

Preface

Notes on CMOS Integrated Circuits & VLSI.

Resources

Some relevant resources:

- EECS 312 - University of Michigan
- EECS 427 - University of Michigan
- [CMOS VLSI Design Web Supplements](#)
 - Contains supplemental materials e.g. lecture slides, figures, solutions, code, etc
- [Digital VLSI Chip Design with Cadence and Synopsys CAD Tools](#)

Textbooks:

- J. Rabaey, A. Chandrakasan, and B. Nikolic. Digital Integrated Circuits A Design Perspective, Edition: 2. Alexandria, VA: Prentice Hall, 2003
- CMOS VLSI Design: A Circuits and Systems Perspective 4th Edition

1 Introduction

1.1 Perspective

i Note 1: Definition - Some definition

Term is defined as blah blah blah...

This note does ...

1.2 High Level Ideas

2 Circuit Basics

A brief review of the fundamental concepts of electrical circuits that form the foundation for understanding CMOS and VLSI design.

2.1 Important Constants

Constant	Symbol	Value	Units
Elementary Charge	e	1.602×10^{-19}	C
Boltzmann Constant	k_B	1.380×10^{-23}	J/K
Room Temperature	T	300	K
Thermal Voltage at 300K	V_T	25.9	mV
Silicon Bandgap	E_g	1.12	eV
Permittivity of Free Space	ϵ_0	8.854×10^{-12}	F/m
Silicon Relative Permittivity	ϵ_r	11.7	-
Silicon Oxide Relative Permittivity	ϵ_{ox}	3.9	-

2.2 Common Unit Conversions

From	To	Conversion
eV	Joules	$1 \text{ eV} = 1.602 \times 10^{-19} \text{ J}$
Temperature	Thermal Voltage	$V_T = \frac{k_B T}{q}$
Frequency	Time Period	$T = \frac{1}{f}$
Resistance \times Capacitance	Time Constant	$\tau = RC$

2.3 Charge, Voltage, Current, Power

2.3.1 Charge (Q)

Electric charge is measured in Coulombs (C). The fundamental unit of charge is the electron charge:

$$Q_e = -1.602 \times 10^{-19} \text{ C}$$

The movement of charge carriers (typically electrons in circuits) creates current.

2.3.2 Voltage (V)

Voltage is the electric potential difference between two points, measured in Volts (V). Key equations:

$$V = IR \text{ (Ohm's Law)}$$

$$V = \frac{dW}{dQ} \text{ (Work per unit charge)}$$

2.3.3 Current (I)

Current is the rate of charge flow, measured in Amperes (A):

$$I = \frac{dQ}{dt}$$

For sinusoidal signals:

$$I = I_0 \sin(\omega t)$$

2.3.4 Power (P)

Power is the rate of energy transfer, measured in Watts (W):

$$P = VI \text{ (instantaneous)}$$

$$P = I^2 R \text{ (resistive loss)}$$

$$P = CV^2 f \text{ (dynamic CMOS)}$$

$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt \text{ (average)}$$

2.4 Resistance, Capacitance, Inductance

2.4.1 Resistance (R)

Resistance is the property of a material that opposes the flow of electric current, resulting in the conversion of electrical energy to thermal energy.

Key equations:

$$V = IR \text{ (Ohm's Law)}$$

$$P = I^2 R \text{ (power dissipation)}$$

$$R = \rho \frac{L}{A} \text{ (bulk resistance)}$$

where:

- ρ is resistivity
- L is length
- A is cross-sectional area

2.4.2 Capacitance (C)

Capacitance (measured in Farads F) is the ability of a component to store electric charge, measured as the ratio of stored charge to the applied voltage. Key equations:

$$\begin{aligned}Q &= CV \text{ (charge stored)} \\I_C &= C \frac{dV}{dt} \text{ (capacitor current)} \\ \tau &= RC \text{ (time constant)}\end{aligned}$$

For parallel plate capacitors:

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

where: - A is plate area - d is plate separation - ϵ_0 is permittivity of free space - ϵ_r is relative permittivity

2.4.3 Inductance (L)

Inductance (measured in Henries H) is the property of a circuit element to oppose changes in current flow by storing energy in a magnetic field:

$$\begin{aligned}V_L &= L \frac{dI}{dt} \\ \tau_L &= \frac{L}{R} \text{ (inductive time constant)} \\ E &= \frac{1}{2} LI^2 \text{ (stored energy)}\end{aligned}$$

2.5 Electric Fields

An electric field is a region of space surrounding a charged particle where another charged particle would experience a force, essentially acting like an invisible “push” or “pull” depending on the charges involved. It is the **force per unit charge** experienced by a small positive test charge placed at that point. Units: V/m or N/C

$$E = \frac{F}{q}$$

-
- electric field is the rate of change of voltage w.r.t. position

- strong electric field -> rapid change in voltage over short distance
- In circuits, voltage sources create electric fields that drive current flow

2.6 KVL & KCL

2.6.1 Kirchhoff's Voltage Law (KVL)

The sum of voltages around any closed loop equals zero:

$$\sum_{k=1}^n V_k = 0$$

2.6.2 Kirchhoff's Current Law (KCL)

The sum of currents entering a node equals the sum of currents leaving it:

$$\sum I_{in} = \sum I_{out}$$

$$\sum_{k=1}^n I_k = 0 \text{ (node equation)}$$

2.7 Basic Circuit Configurations

2.7.1 Series Connections

In series connections, components share the same current:

$$I_{total} = I_1 = I_2 = \dots = I_n$$

For components in series:

- Resistors: $R_{total} = R_1 + R_2 + \dots + R_n$
- Capacitors: $\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$
- Inductors: $L_{total} = L_1 + L_2 + \dots + L_n$
- Voltage Division: $V_i = V_{total} \frac{R_i}{R_{total}}$

2.7.2 Parallel Connections

In parallel connections, components share the same voltage:

$$V_{total} = V_1 = V_2 = \dots = V_n$$

For components in parallel:

- Resistors: $\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$
- Capacitors: $C_{total} = C_1 + C_2 + \dots + C_n$
- Inductors: $\frac{1}{L_{total}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$
- Current Division: $I_i = I_{total} \frac{R_{total}}{R_i}$

2.8 Capacitor

A capacitor stores electrical energy in an electric field created between two conductive plates separated by an insulator (dielectric)

- When a voltage is applied, electrons build up on one plate (creating negative charge), and the other plate loses electrons (resulting in positive charge)
-

2.9 Additional Topics Relevant to CMOS/VLSI

2.9.1 Small Signal Analysis

Key parameters and equations:

$$g_m = \frac{\partial I_D}{\partial V_{GS}} \text{ (transconductance)}$$

$$r_o = \frac{\partial V_{DS}}{\partial I_D} \text{ (output resistance)}$$

$$A_v = -g_m r_o \text{ (small-signal gain)}$$

2.9.2 RC Networks

Time domain analysis:

$$v(t) = V(1 - e^{-t/RC}) \text{ (charging)}$$

$$v(t) = Ve^{-t/RC} \text{ (discharging)}$$

$$t_p \approx 0.69RC \text{ (propagation delay)}$$

2.9.3 Noise and Signal Integrity

Thermal noise power spectral density:

$$S_v(f) = 4k_BTR \text{ (V}^2/\text{Hz)}$$

Shot noise current spectral density:

$$S_i(f) = 2qI_D \text{ (A}^2/\text{Hz)}$$

Signal-to-Noise Ratio:

$$SNR = \frac{P_{signal}}{P_{noise}} = \frac{V_{signal,rms}^2}{V_{noise,rms}^2}$$

2.9.4 Semiconductor Physics Basics

Carrier concentration:

$$n_i^2 = N_C N_V e^{-E_g/k_B T}$$

Built-in potential:

$$V_{bi} = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$$

MOSFET threshold voltage:

$$V_{th} = V_{FB} + 2\phi_F + \frac{\sqrt{2\epsilon_s q N_A (2\phi_F)}}{C_{ox}}$$

where:

- V_{FB} is the flatband voltage
- ϕ_F is the Fermi potential
- N_A is acceptor concentration
- C_{ox} is oxide capacitance per unit area

2.10 PN Junctions

The PN junction is fundamental to semiconductor devices and CMOS operation. Key concepts and equations:

2.10.1 Built-in Potential

The built-in potential (V_{bi}) across the junction at equilibrium:

$$V_{bi} = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$$

where:

- N_A is acceptor concentration in p-region
- N_D is donor concentration in n-region
- n_i is intrinsic carrier concentration
- V_T is thermal voltage ($k_B T/q$)

2.10.2 Depletion Region

The depletion width (W) under bias:

$$W = \sqrt{\frac{2\epsilon_s}{q} \left(\frac{N_A + N_D}{N_A N_D}\right) (V_{bi} - V_A)}$$

where:

- V_A is the applied voltage
- ϵ_s is semiconductor permittivity
- q is elementary charge

2.10.3 Current-Voltage Relationship

The ideal diode equation:

$$I_D = I_S (e^{V_D/V_T} - 1)$$

where:

- I_S is the reverse saturation current
- V_D is the diode voltage
- V_T is thermal voltage

The saturation current:

$$I_S = qA\left(\frac{D_p}{L_p}p_n + \frac{D_n}{L_n}n_p\right)$$

where:

- D_p, D_n are diffusion coefficients
- L_p, L_n are diffusion lengths
- A is junction area

2.10.4 Junction Capacitance

The junction capacitance has two components:

Depletion capacitance:

$$C_j = \frac{C_{j0}}{\sqrt{1 - V_D/V_{bi}}}$$

Diffusion capacitance:

$$C_d = \tau_T \frac{dI_D}{dV_D} = \tau_T \frac{I_D + I_S}{V_T}$$

where:

- C_{j0} is zero-bias junction capacitance
- τ_T is transit time

2.10.5 Temperature Effects

Temperature dependence of key parameters:

$$I_S(T) \propto T^3 e^{-E_g/k_B T}$$

$$V_{bi}(T) = V_{bi}(T_0) - \beta(T - T_0)$$

where β is the temperature coefficient.

2.11 Note

i Note on Temperature Dependencies

Many parameters in CMOS circuits have significant temperature dependencies. Key relationships include:

- Mobility: $\mu(T) \propto T^{-3/2}$

- Threshold voltage: $V_{th}(T) = V_{th}(T_0) + \alpha(T - T_0)$
- Leakage current: $I_{leak} \propto T^2 e^{-E_g/2k_B T}$

3 High-level Overview

3.1 MOS Transistors

Silicon Lattice

PN Junction

NMOS PMOS

3.2 CMOS Logic

3.2.1 Pass Transistors, Transmission Gates

3.2.2 Tristates

3.2.3 Multiplexers

3.3 Sequential Circuits

3.3.1 Latches

3.3.2 Flip-Flops

3.4 Fabrication & Layout

3.4.1 Fabrication Process

3.4.2 Layout Design Rules

3.4.2.1 Gate Layout

3.4.2.2 Stick Diagrams

3.5 Design Partitioning

3.6 Architecture

3.7 Logic Design

3.8 Circuit Design

3.9 Physical Design

3.10 Design Verification

3.11 Fabrication, Packaging, and Testing

4 CMOS Basics

4.1 MOS Transistor Basics

4.1.1 Silicon Lattice

Silicon (Si)

- semiconductor, forms basic starting material
- A Group IV element -> forms covalent bonds with 4 adjacent atoms
 - with **pure silicon**, all valence electrons are in chemical bonds, thus a **poor conductor**
- Raise conductivity adding **dopants** into the lattice (adding impurities)
- Dopant from Group V (e.g. arsenic As) has 5 valence electrons
 - Replacing one silicon atom leads to the lattice having 4 bonds but 1 valence electron loosely bound (b in fig. below)
 - Free electron can carry current thus raising conductivity
 - This is an **n-type** semiconductor
 - * Free **carriers** are **negatively charged electrons**
- Dopant from Group III (e.g. boron B) has 3 valence electrons
 - Similarly, boron atom can borrow electron from neighboring Si which is now short by one electron
 - * This creates a **hole** (a missing electron)
 - * hole acts as positive carrier
 - This is a **p-type** semiconductor (c in fig. below)
- Note that when current flows, electrons and holes move in **opposite directions**
 - Recall how electrons move opposite to direction of conventional current flow
 - * Holes move in same direction as conventional current flow
 - * in semiconductors, current can be carried by holes as well because both electrons and holes are primary charge carriers
 - This goes into band structure of semiconductors:

- Electrons occupy two main energy bands: **valence band** (lower energy) and **conduction band** (higher)
- When an electron gains enough energy (eg through doping) it moves from valence to conduction band, leaving a hole in valence band
- p-type doping creates deficit of electrons in valence band (creating holes)

 


Figure 4.1: Silicon lattice shown as 2D plane for simplicity (but is actually 3D cubic crystal).
Source: (Weste and Harris 2010)

4.1.2 PN Junction

 


Figure 4.2: PN Junction. Source: (Weste and Harris 2010)

Junction between p-type (anode) and n-type (cathode) is a **diode**

- Voltage on p-type $>$ n-type: diode is **forward biased** and current flows
- Otherwise (p-type \leq n-type): diode is **reverse biased**, very little current flows

 


Figure 4.3: [Source](#)

- charge transfer (of electrons and holes) across the junction is called **diffusion**
- free electrons in the anode fills up some holes in the cathode
- this forms a **depletion layer**
 - depletion layer is depleted of any free carriers (electrons or holes)
 - * in comparison on the n- and p-regions there are still free carriers
 - acts as a barrier to further current flow
- When applying **forward bias** (anode has higher voltage)
 - Positive voltage on p-type pushes holes towards junction
 - Negative voltage on n-type pushes electrons towards junction (where negative ions are repelling)
 - Shrinks depletion region
 - * Once voltage is high enough, depletion region becomes so thin that electrons can freely pass (current flow)
- When applying **reverse bias** (anode has lower voltage)
 - Negative voltage on p-type pulls holes away from junction
 - Positive voltage on n-type pulls electrons away from junction
 - Makes depletion region wider
 - * Creates stronger barrier to current flow

Analogy: A hill between two valleys. Forward bias reduces height of the hill, making it easy for charges to cross the hill. Reverse bias makes the hill taller, making it more difficult.

Why does the depletion region create a barrier? Why don't more electrons cross into p-type to fill up holes?

- When an electron fills a hole in the p-type
 - leaves behind positive ion on n-type (an atom lost its extra electron)
 - leaves behind a negative ion on the p-type (an atom has an extra electron)
- Thus depletion region becomes filled with positive ions on n-type side and negative ions on p-type side
 - Recall that ions are charged particles - (i.e. has more electrons than protons, or more protons than electrons)
- **Ions create an electric field**
 - (+) ions in the n-side and (-) ions in the p-side create an electric field pointing from n to p
 - * electric field opposes the further flow of electrons
 - * Think of like building static electricity: more charge separates, the stronger the opposing force becomes

 


Figure 4.4: [Source](#)

4.1.3 Transistor Structure

Terminology clarifications:

- Metal-Oxide Semiconductor (MOS) - refers to the structure used in MOSFETs (ie consisting of the M, O, and S)

- Metal-Oxide Semiconductor Field-Effect Transistor (MOSFET) - the actual type of FET that uses MOS structure for a transistor
- Field-Effect Transistors (FET) - superset of MOSFET - transistors that control current using an electric field
 - Voltage-controlled device
 - Sometimes used interchangeably with MOSFET
- Complementary Metal-Oxide Semiconductor (CMOS) - refers to the technology that use both NMOS and PMOS (complementary)
 - Why CMOS?
 - * In steady-state, only one type of transistor (N or PMOS) conducts
 - Thus no direct current path from supply to ground, leading to lower static power
 - i.e. power mainly comes from switching (although see further notes on static power)
 - * Full rail-to-rail swing (0 to VDD) - good logic level separation
 - E.g. compared to pure NMOS logic, CMOS has lower static power dissipation and full voltage swing (but slower)

FET because transistor operation is controlled by electric fields (thus the *field effect* transistor)

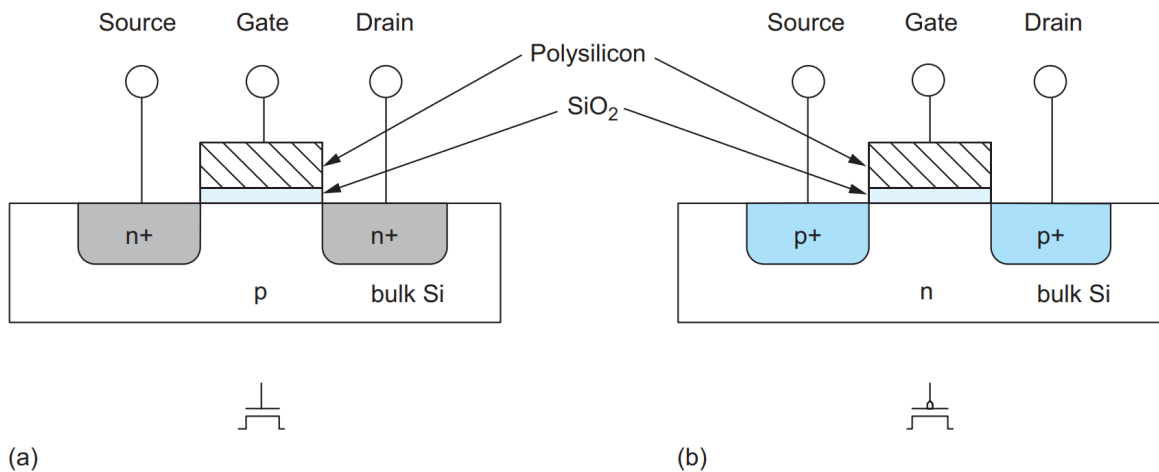


Figure 4.5: Cross-sections of a) nMOS, and b) pMOS. n+/p+ regions are heavily doped.
Source: (Weste and Harris 2010)

CMOS technology provides two types of transistors/devices: **n-type transistor (nMOS)**, and **p-type transistor (pMOS)**

MOS Structure:

- **gate** - conducting gate
 - Early transistors: metal gates
 - 1970s and on: **polysilicon** (polycrystalline silicon)
 - metal gates have reemerged in '07
- **silicon dioxide** (SiO_2 , glass)
 - Essentially works as the dielectric (insulator) between gate and semiconductor
- **substrate/body/bulk** - the silicon wafer
- NMOS is built with p-type body, with n-type semiconductor adjacent to the gate. These regions are the **source** and the **drain**. The body is typically grounded.
 - PMOS is opposite
- The substrate is either n-type or p-type, with the other flavor of transistor built in a special **well** to form the body of the opposite type
- **gate** is the control input - affecting flow of electrical current between source and drain

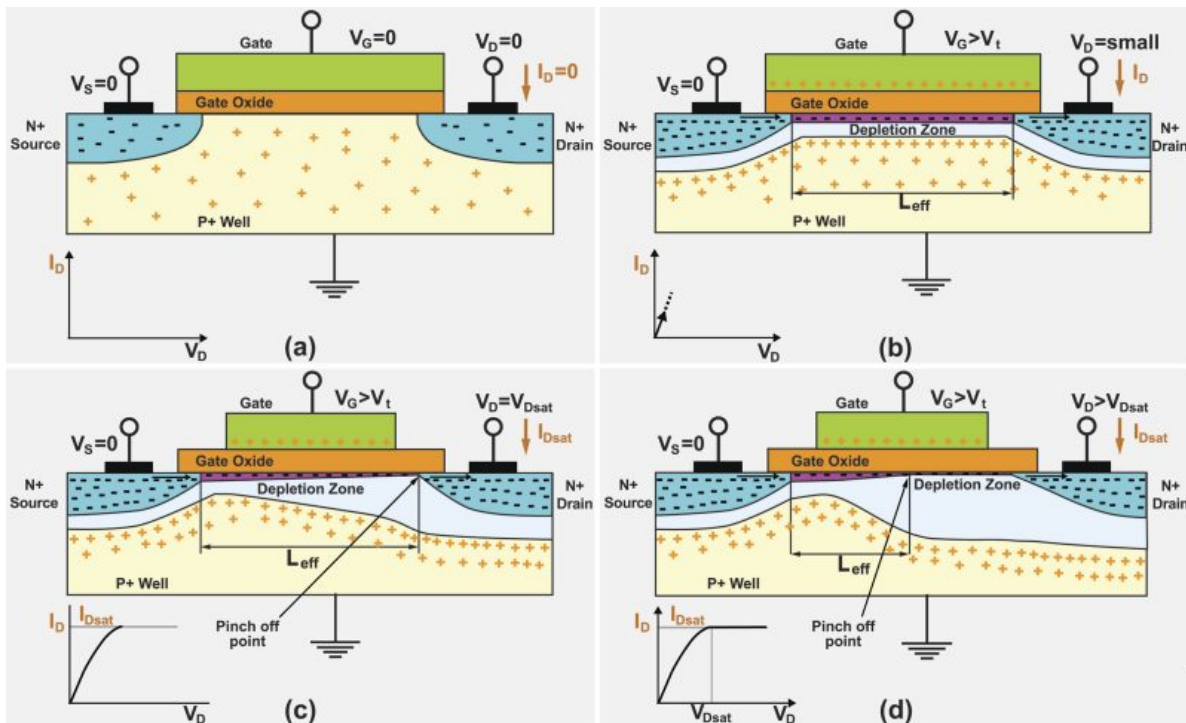



Figure 4.6: NMOS Operations. [Source](#)

NMOS:

- body is grounded (pn junction of source and drain to body is reverse-biased)
 - If gate is also grounded, no current can flow through the junctions since they are reverse-biased
 - * Thus transistor is OFF
 - As gate voltage is raised, gate creates electric field that attracts free electrons
 - * Why does raising gate voltage attract free electrons?
 - MOS structure essentially creates a parallel-plate capacitor (gate as a plate, and silicon beneath SiO₂ as a plate)
 - Gate voltage (potential difference) between the two plates create an electric field
 - Since SiO₂ is an insulator, charge cannot flow through it, thus inducing charge redistribution in the semiconductor
 - Positive gate voltage -> “capacitor” of gate and substrate forms electric field pointing downwards, pulling electrons upwards (positive potential of gate attracts them)
 - Once voltage is raised enough, electrons outnumber holes and creates a **channel**
 - * **channel** is the thin region under the gate that becomes inverted to act as an n-type semiconductor
 - allowing conducting path of electron flow between source and drain
 - Thus transistor is ON

PMOS:

- Situation is opposite: body is at positive voltage
 - When gate is at positive voltage, source and drain junctions are reverse-biased -> no current flow
 - At lowered gate voltage, positive charges attracted towards the bottom of the SiO₂
 - * Low enough gate voltage inverts the channel creating a conducting path for positive carriers from source to drain
- High voltage (Logic level 1) usually denoted V_{DD} or POWER
 - VDD for Voltage Drain Drain
- Low voltage (Logic level 0) called GROUND (GND) or denoted as V_{SS}
 - VSS for Voltage Source Source
- This allows MOSFETs to be viewed as ON/OFF switches

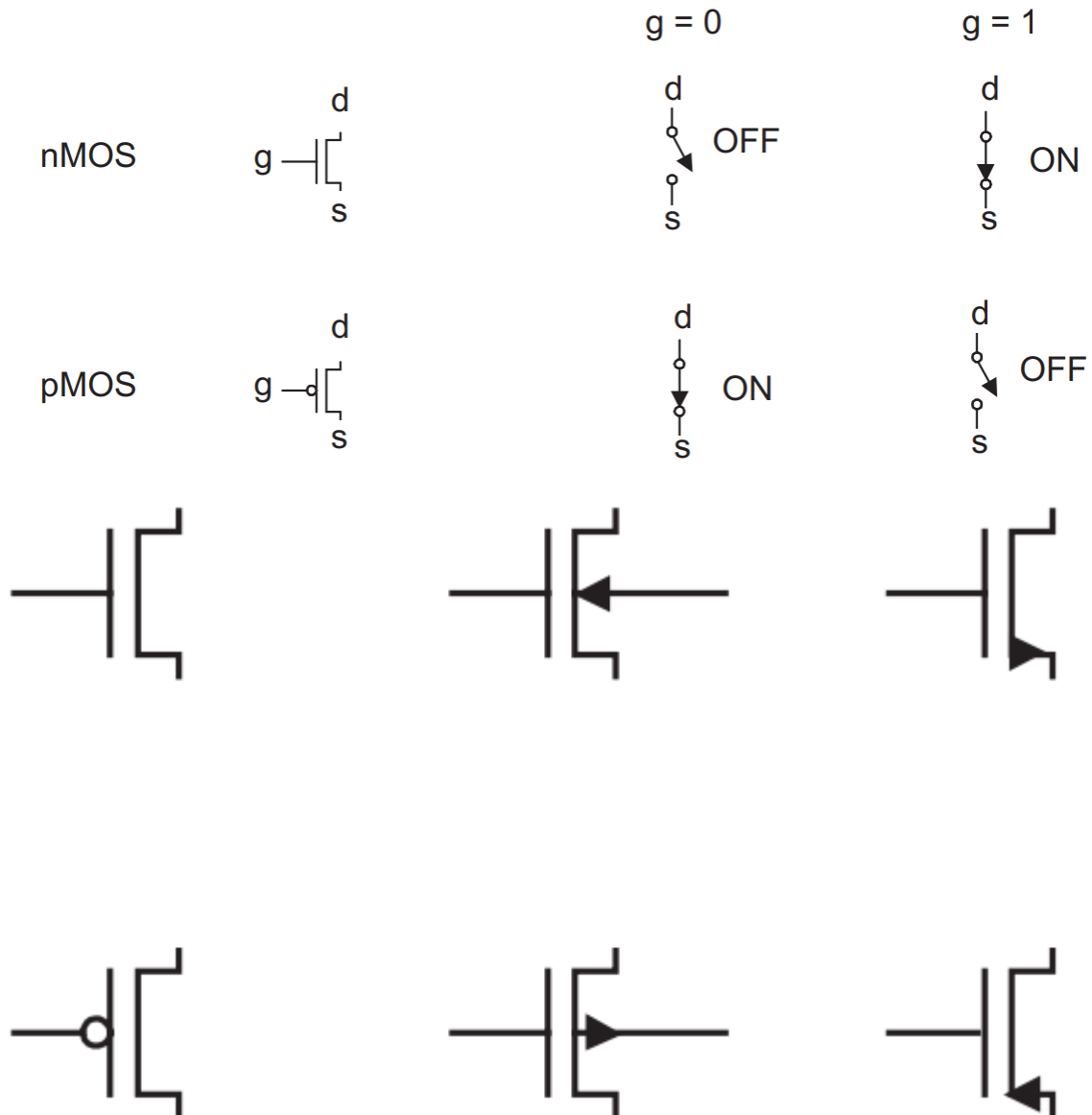

- The MOS transistor is a **majority-carrier** device - gate voltage controls current in a conducting channel between source and drain
 - NMOS: majority carriers are electrons
 - PMOS: majority carriers are holes
- Note that the source terminal sources the majority carrier which go to the drain
 - i.e. for nmos electrons go from source to drain, for pmos holes go

4.1.4 Very Simplified Model

The following demonstrates a very simplified MOS without the source and drain:

 


FIGURE 2.2 MOS structure demonstrating (a) accumulation, (b) depletion, and (c) inversion

Figure 4.7: Source:(Weste and Harris 2010)

- a) negative voltage on gate - holes attracted to region beneath the gate
- b) small positive voltage on gate - some positive charge on the gate, repelling the like holes below the gate

- **depletion** region - region in the body where holes are repelled away
- c) higher positive potential larger than a threshold voltage V_t on gate - attracts a lot of positive charge to the gate, further repelling the holes and some free electrons in the body are attracted to the region beneath the gate
- **inversion** layer - the conductive layer of electrons in the p-type body

Now let us examine an NMOS:

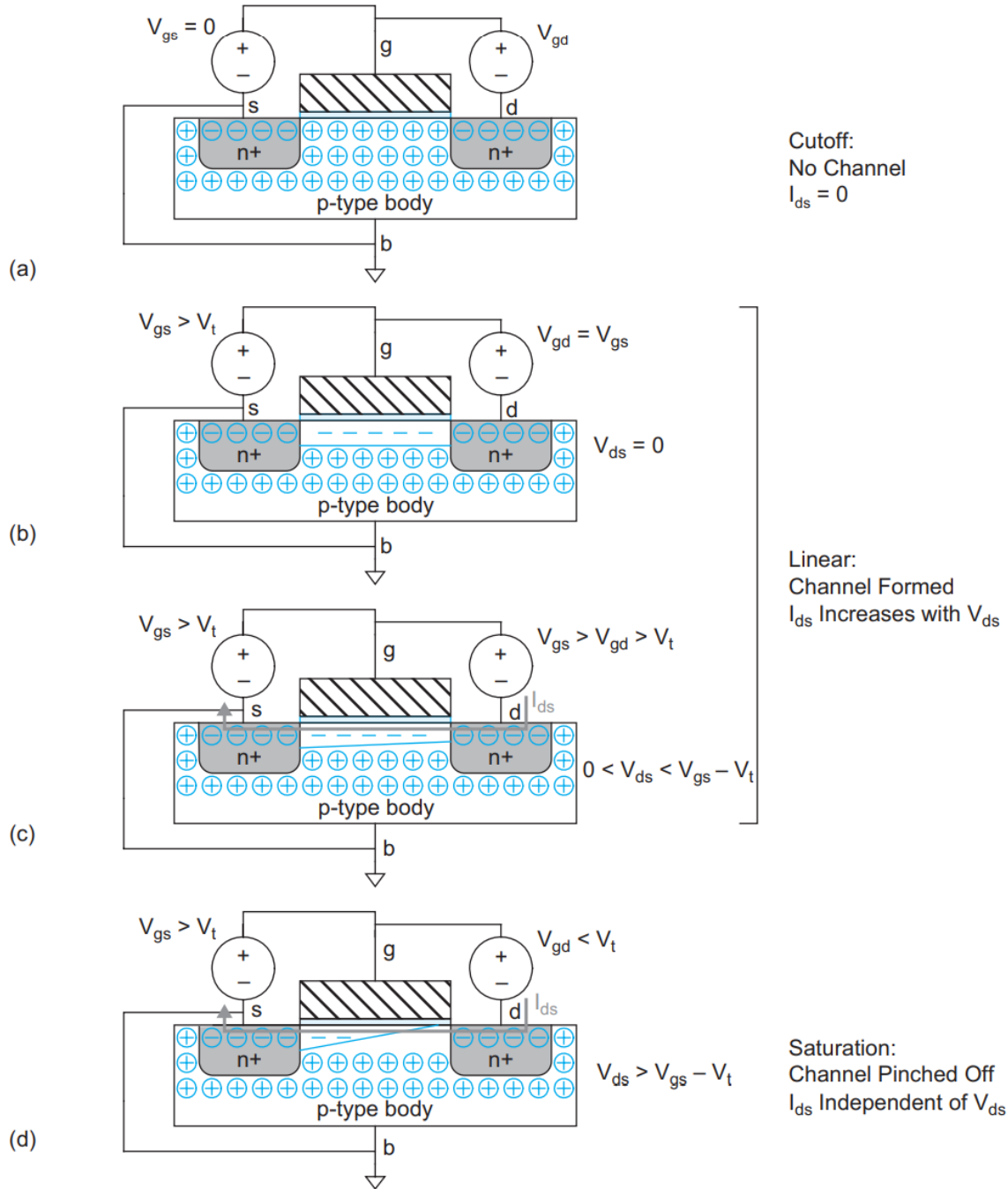


Figure 4.8: NMOS Regions of Operation: a) Cutoff region b, c) Linear region d) Saturation region Source: (Weste and Harris 2010)

Cutoff Region:

- $V_{gs} < V_t$
- Source and drain have free electrons, body has free holes but no free electrons
 - junction between body and source/drain are zero/reverse-biased, so little to no current flow
 - OFF
-

Linear Region:

- aka resistive, triode, nonsaturated, unsaturated, ohmic
- $V_{gs} > V_t$
 - but $0 < V_{ds} < V_{gs} - V_t$
- Inversion region of majority carriers (in this case electrons) - named the **channel** - creates a conductive path between source and drain
- ON
- Number of carriers and conductivity increases with gate voltage
- **Potential difference between drain and source:** $V_{ds} = V_{gs} - V_{gd}$
 - if V_{ds} is 0, no electric field to push current from drain to source
- When small positive V_{ds} - current I_{ds} flows from drain to source
 - The current increases with both V_{ds} and V_{gs}

Saturation Region:

- V_{ds} is so large that $V_{gd} < V_t$
- channel is no longer inverted and is **pinched off**

Analogy: water valve

- Gate is the valve of a water pipe

4.2 Long-Channel I-V Characteristics

4.3 C-V Characteristics

4.4 Nonideal I-V Effects

4.5 DC Transfer Characteristics

4.6 Resources / References

Videos:

- [CircuitBread - MOSFET](#)
- [CircuitBread - FET Regions of Operation](#)

5 CMOS Fabrication & Process Technology

6 CMOS Capacitance

7 Inverters and More Gates

8 Delay

9 Power

10 Interconnect

11 Robustness

12 Circuit Simulation

13 Combinational Circuit Design

Ref (cmosvlsi-4th?)

14 Sequential Circuit Design

15 Datapath Subsystems

16 Array Subsystems

17 Special-Purpose Subsystems

18 Design Methodology and Tools

19 Testing, Debugging, and Verification

20 Summary

In summary...

21 Interview & Problems

21.1 Interview

Concepts to know:

21.2 Problems

Common interview problems:

21.2.1 CMOS

21.2.2 Logic Design

References

Weste, Neil, and David Harris. 2010. *CMOS VLSI Design: A Circuits and Systems Perspective*. 4th ed. USA: Addison-Wesley Publishing Company.